

Complete the missing information from the circuit: (14 marks)

