

Name:______Date Due: <u>Tuesday, April 14, 2020</u> Mark: [APPL: /10]

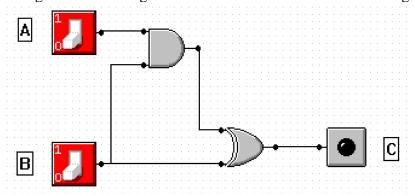Using MultimediaLogic construct truth tables for the following circuits.



INP	UTS	OUTPUT
Α	В	С
0	0	
0	1	
1	0	
1	1	

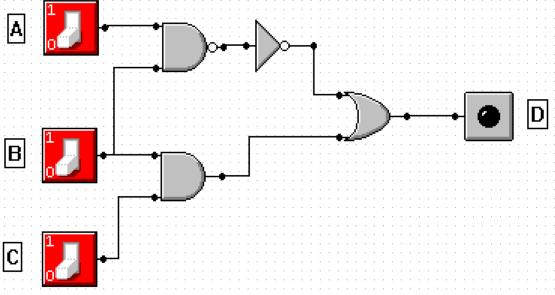

INPUTS			OUTPUT
A	В	C	D